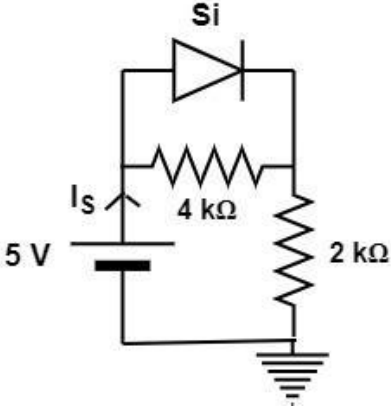
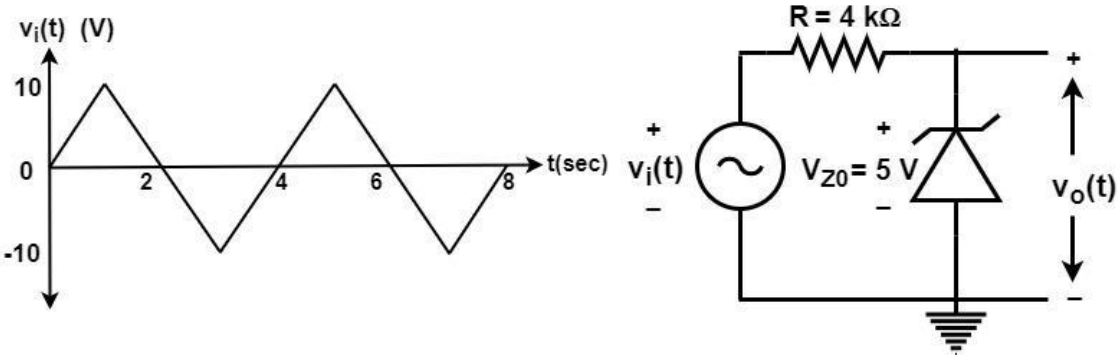
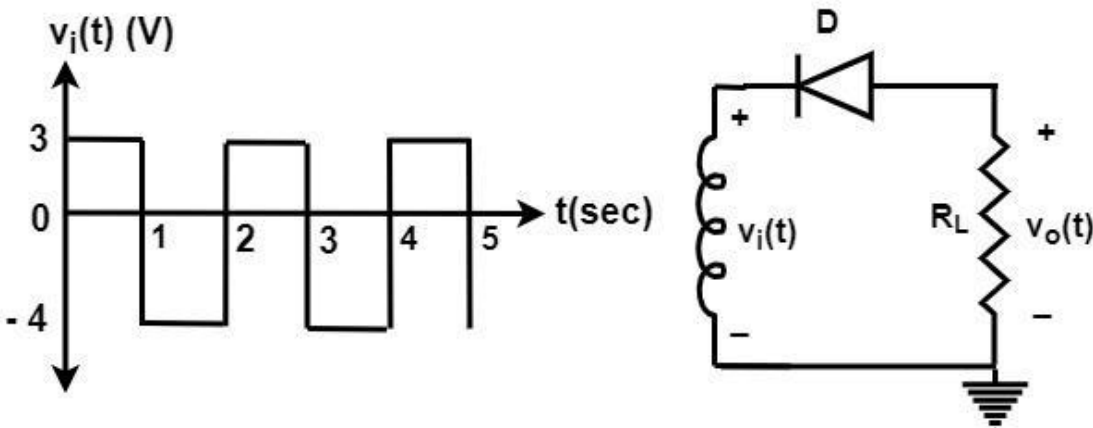




National Institute of Technology, Silchar
Mid-Semester (UG) Examinations, January- 2022

Subject Code: EC101
Semester: First
Duration: One Hour

Subject: Basic Electronics
Department: ECE, CSE & EE
Total Marks: 20

All Questions Are Compulsory

Q. No.	Questions	Marks
1	<p>Find the current(I_S) supplied by the 5V battery in the circuit shown in the below figure.</p> 	3
2	<p>Analyze the circuit shown in the below figure and draw the output waveform $v_o(t)$ of it corresponding to the given input signal if the Zener diode is made up of Si($V_Z = 0.7V$).</p> 	3
3	<p>Determine the ripple factor of the output of the rectifier circuit for the input signal as shown in the figure below considering the ideal diode.</p> 	2

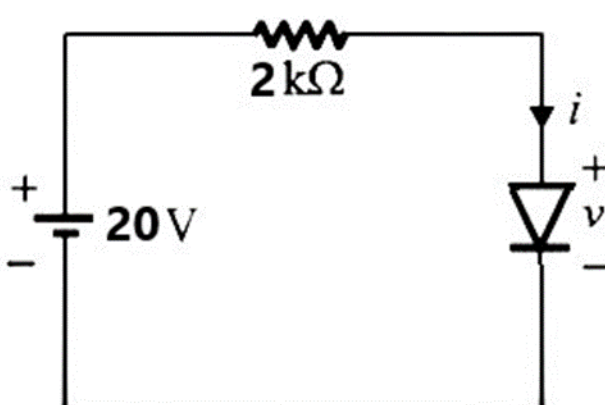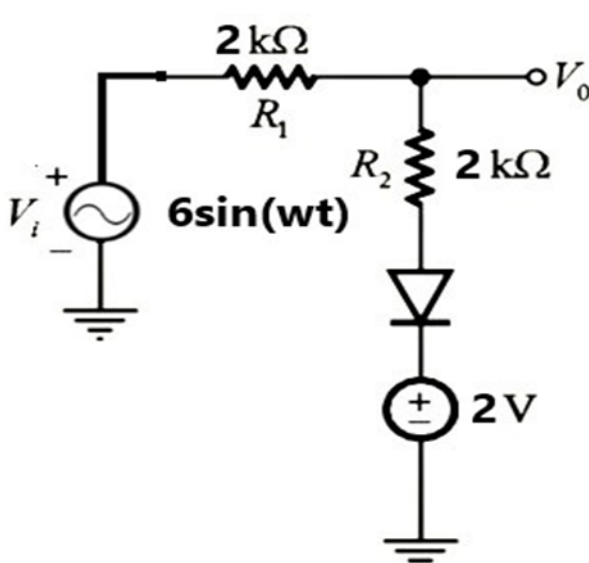4	<p>The i-v characteristics of diode in the circuit given below are</p> $i = \begin{cases} \frac{v-0.7}{700} \text{ A} & v \geq 0.7 \text{ V} \\ 0 & v < 0.7 \text{ V} \end{cases}$ <p>Determine the current i in the circuit.</p> 	3
5	<p>The diode in the circuit shown is Ge (cut in voltage 0.3 V). if $V_i = 6 \sin \sin (wt) \text{ volt}$, then determine minimum and maximum values of V_o (in volts).</p> 	3
6	<p>Explain how a Zener diode can be used to act as voltage regulator with a suitable circuit diagram.</p>	3
7	<p>Draw the IV characteristics of a normal PN junction diode and a Zener diode together in a single plot to highlight their differences and explain the reasons behind those differences.</p>	3

*****END*****