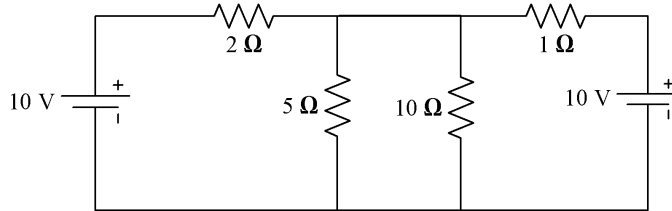


## Module: 3 : Network Theorem


### Tutorial Sheet Set 1

#### THEVENIN'S THEOREM


1. In the below network, find the current flowing through the  $10\ \Omega$  resistor utilising Thevenin's theorem. [ Ans:  $I = 1.2\text{ A}$  ]



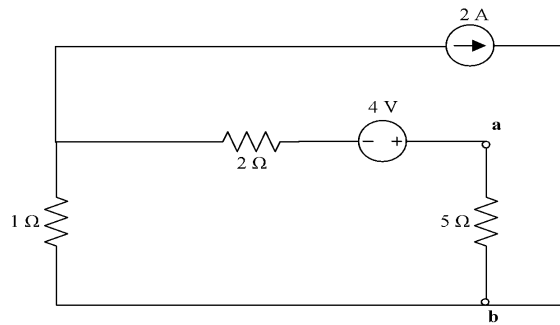
2. In the below circuit, find the power loss in  $r_L = 5\ \Omega$  utilising Thevenin's theorem. [ Ans:  $P_L = 0.31\text{ W}$  ]



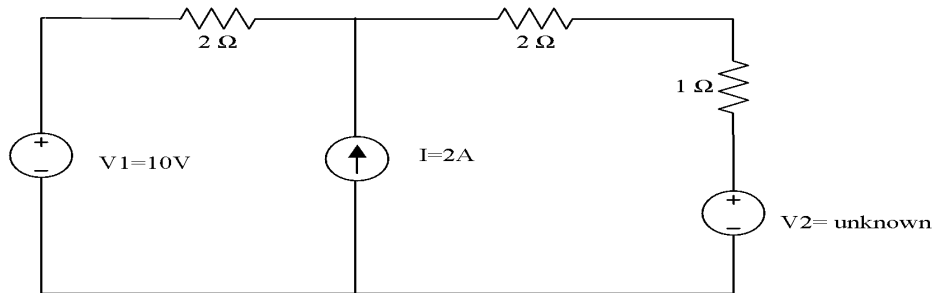3. Find Thevenin's voltage across a-b terminal in the circuit of below fig. Also find the internal resistance across open circuit a-b terminal. [ Ans:  $V_{th} = \quad$ ,  $R_{th} = \quad$  ]




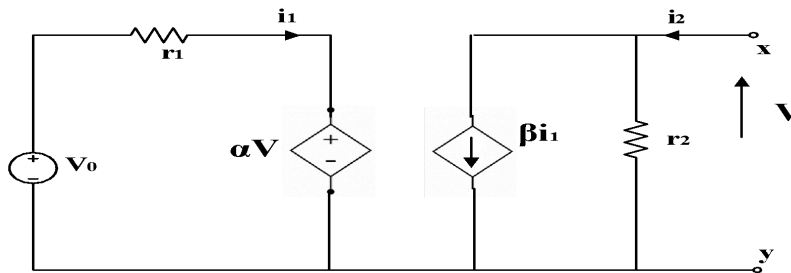4. Find the Thevenin's equivalent impedance of the given circuit in fig. Looking from x-y terminals. [ Ans:  $Z_{int} = r_1 / (r_1 - r_2)$  ]



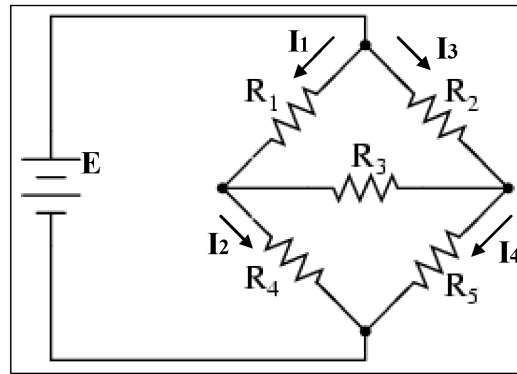
5. Thevenised the bridge circuit across a-b in figure.

[Ans:  $R_{int} = (r_1 r_2 r_3 + r_1 r_2 r_3 + r_1 r_2 r_3 + r_1 r_2 r_3) / ((r_1 + r_2)(r_2 + r_3))$  ]




6. Obtain Thevenin's equivalent circuit across x-y in the figure.

[ $R_{th} = 4 \Omega$ ]

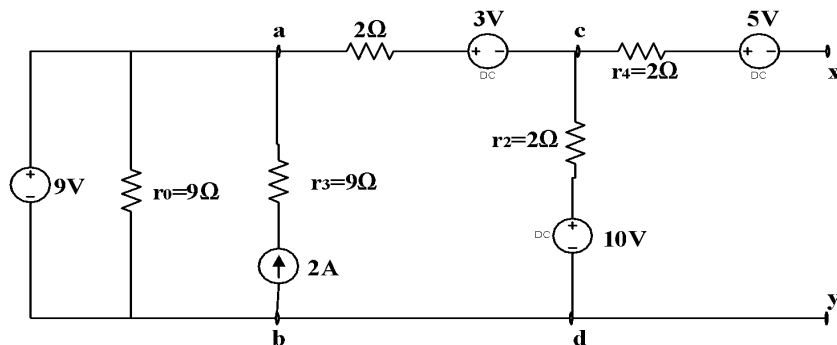

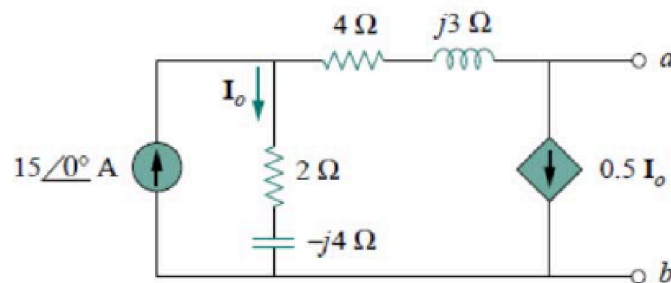
7. Find the Thevenin equivalent of the circuit in Fig as seen from terminals a-b.

[Ans:  $V_{th} = 55 \angle -90^\circ \text{ V}$ ,  $Z_{th} = 4 - j0.6667 \Omega$ ]




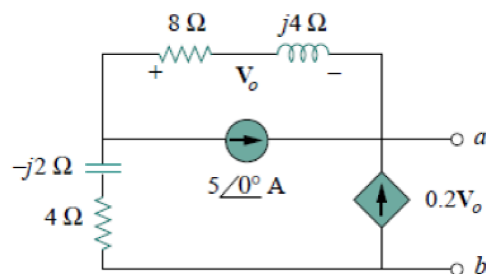8. Determine the Thevenin equivalent of the circuit in Fig. as seen from the terminals a-b. [Ans:


$Z_{th} = 12.166 \angle 136.3^\circ \Omega$ ,  $V_{th} = 7.35 \angle 72.9^\circ \text{ V}$ ]



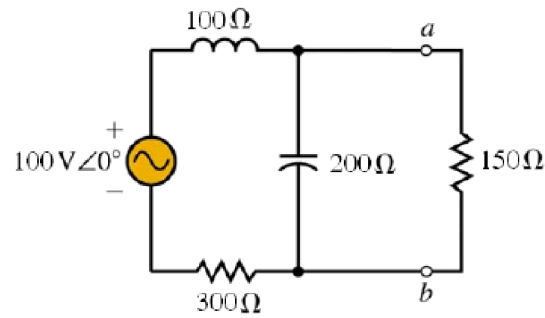9. Convert the source below into a Thèvenin equivalent and determine the current  $I_{ab}$  through the load resistor.




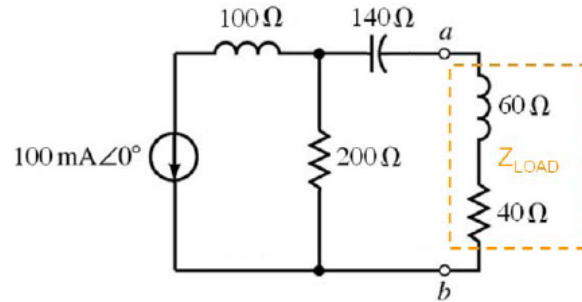10. Convert the source below into a Thévenin equivalent.



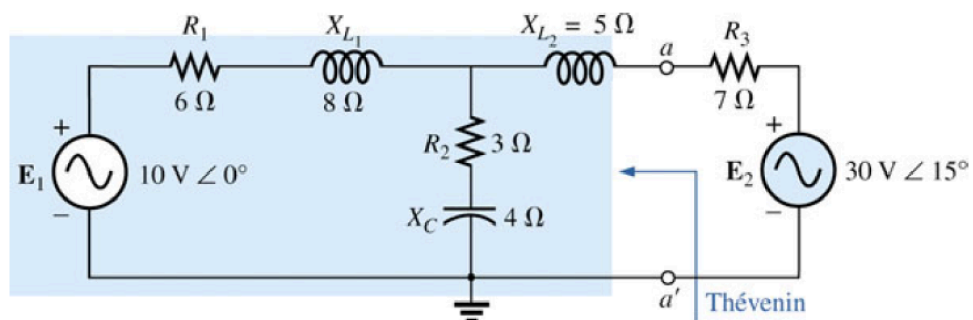
11. Find the Thevenin equivalent circuit for the network external to the branch  $a-a'$ .

[Ans: Boylestad, *Introductory Circuit Analysis*, 12th ed., Prentice Hall, 2010]




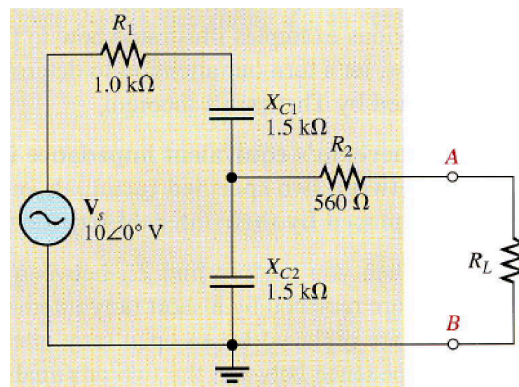12. For the circuit in below Figure, determine the Thevenin voltage as seen by  $R_L$ .

[Ans:  $V_{th} = 4.75 \angle -18.4^\circ$ ]




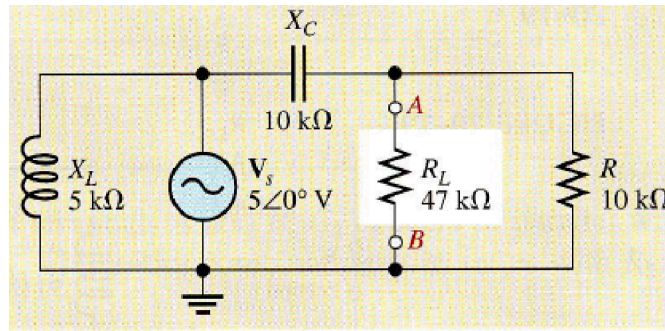13. For Figure, find  $V_{th}$  for the circuit external to  $R_L$ . [Ans:  $3.54 \angle 45^\circ$ ]




## SUPERPOSITION THEOREM

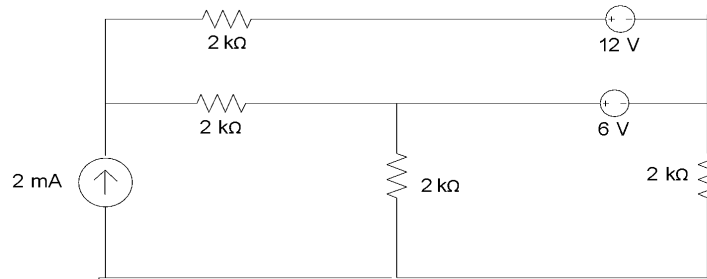1. Use superposition to find  $i_o$  in the circuit in figure. [Ans:  $i_o = 2.5\text{ mA}$ ]




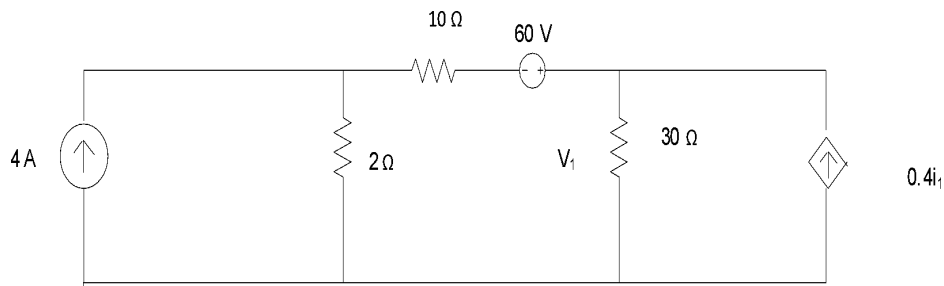2. Find the voltage  $V_1$  using the superposition principle. [Ans:  $V_1 = 82.5\text{ V}$ ]




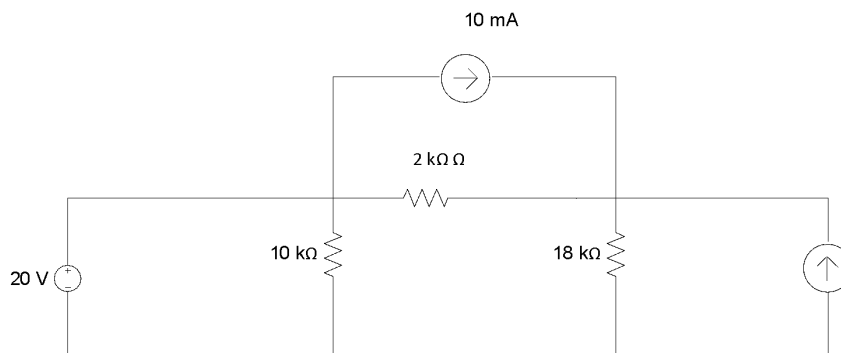3. Refer to the circuit shown below. Before the 10 mA current source is attached to terminals x-y, the current  $i_a$  is found to be 1.5 mA. Use the superposition theorem to find out the value of  $i_a$  after the current source is connected.


Verify your solution by finding  $i_a$ , when all the three source are acting simultaneously.  
[ Ans:  $i_a =$  ]



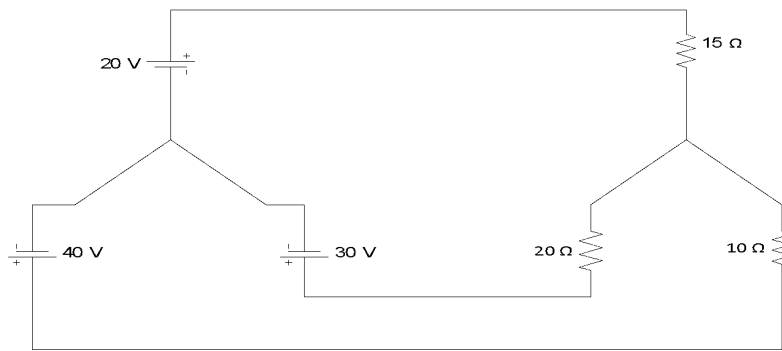
4. Using superposition theorem, find the current in each branch of the network shown. [Ans. -0.768, -0.074, -0.842]



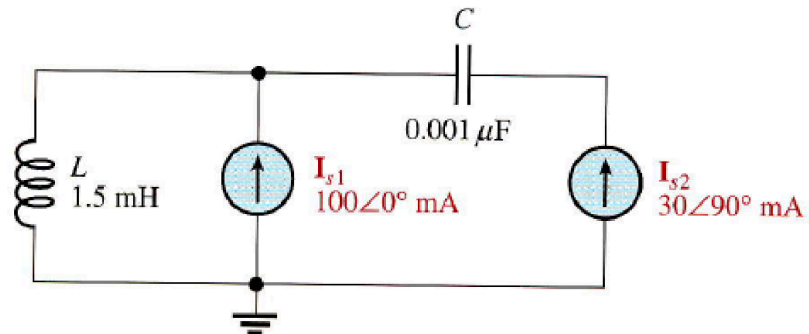
5. Find the coil current in Figure. Assume the sources are ideal [Ans:  $104 \angle 16.70^\circ$  mA]



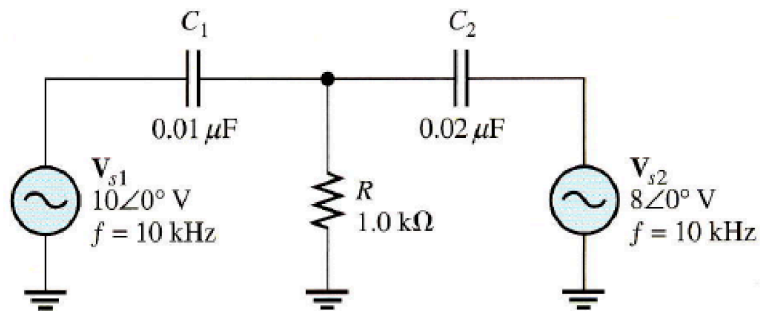6. Find the current in R of Figure internal source impedances are zero. using the superposition theorem. Assume the internal source impedances are zero. [Ans:  $I_R = 7.64 \angle 27.9^\circ$  mA]



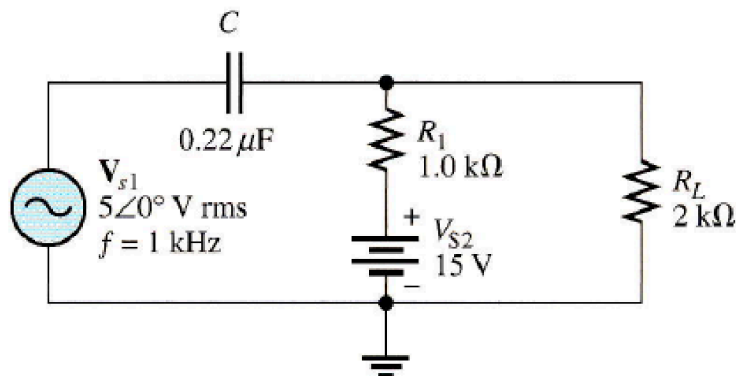7. Find the total current (by using Superposition Theorem) in the resistor  $R_L$  in Figure. Assume the sources are ideal. [Ans:  $1.69 \angle 47.3^\circ$  mA]



## MAXIMUM POWER TRANSFER THEOREM

- Find the value of  $R$  in the circuit of fig.1 such that maximum power transfer takes place. What is the amount of this power? [ Ans:  $R_{th} = 0.85 \Omega$ ,  $P_{max} = 12 \text{ W}$  ]

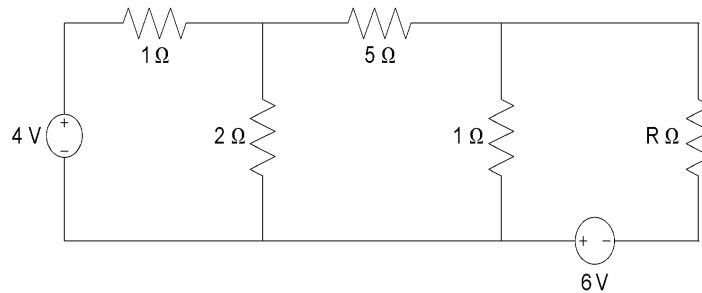


Fig. 1.

- What should be the value of  $R$  such that maximum power transfer can take place from the rest of the network to  $R$  in the fig.2? Obtain the amount of this power. [ Ans:  $R = 5.33 \Omega$ ,  $P_{max} = 188 \text{ mW}$  ]

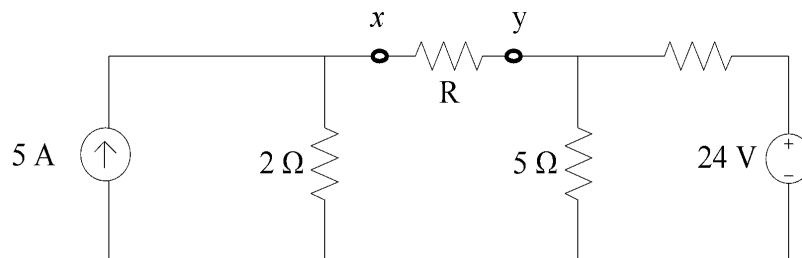


Fig. 2.

- What resistance should be connected across x-y in the circuit shown in fig.3 such that maximum power is developed across this load resistance? What is the amount of this maximum power? [ Ans:  $R_{th} = 421/65 \Omega$ ,  $P_{max} = 3.34 \text{ W}$  ]

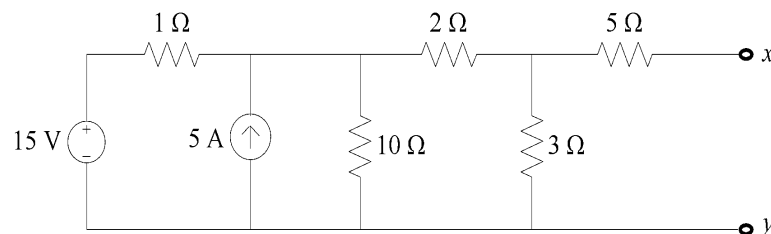


Fig. 3.

- Find  $R$  to have maximum power transfer in the circuit of fig.4. Also obtain the amount of maximum power. [ Ans:  $R_{th} = 1.765 \Omega$ ,  $P_{max} = 19.221 \text{ W}$  ]

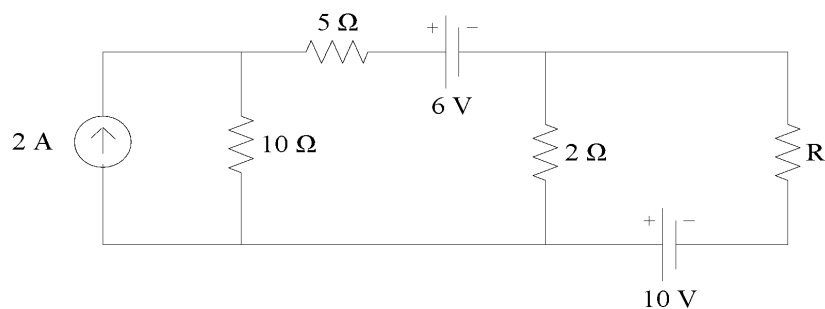


Fig. 4.

5. Assuming maximum power transfer find the source to R, find the value of this amount of power in the circuit of fig. 5. [ Ans:  $R = 8.33 \Omega$ ,  $P_{\max} = 33.34 \text{ W}$ ]


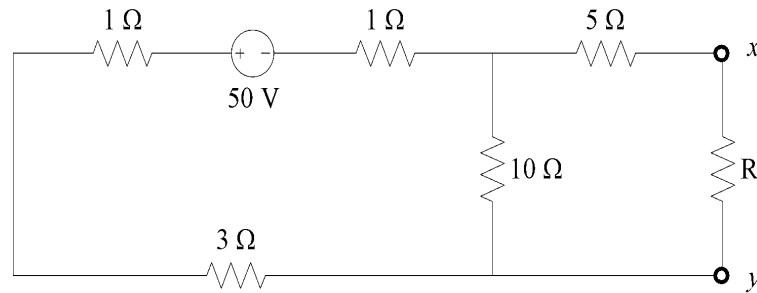



Fig. 5.

### NORTON'S THEOREM

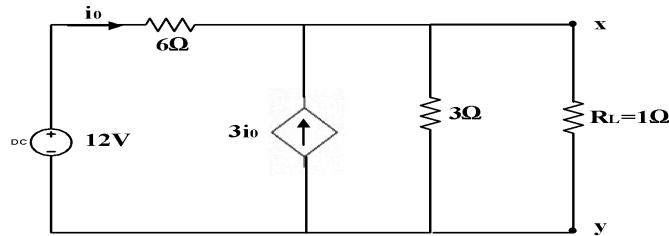1. Find the current through  $R_L$  in the circuit shown below using Norton's theorem. [ Ans:  $I = 4 \text{ A}$ ]




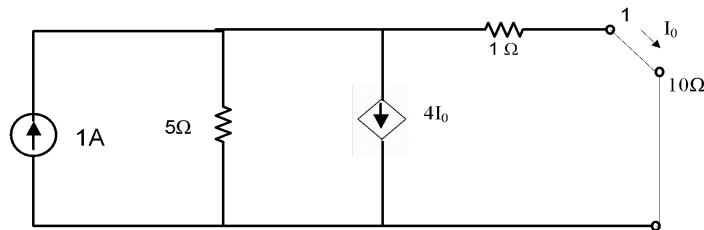2. Find the power loss in  $10 \Omega$  resistor in the circuit of below fig. Using Norton's theorem. [ Ans:  $P_L = 0.195 \text{ W}$ ]




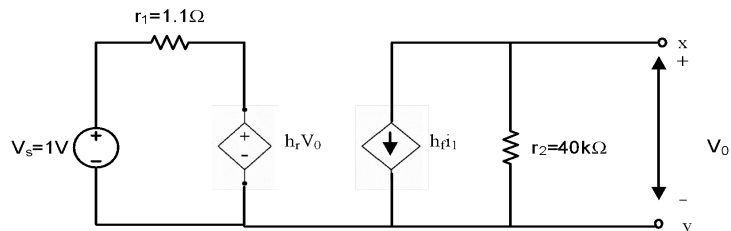3. Find Norton's equivalent to the left of x-y terminals for the CE configuration of transistor equivalent circuit shown in fig. Assume  $h_r = 2 \times 10^{-4}$ ;  $h_f = 50$ .


[ Ans:  $R_{\text{int}} = 62.82 \text{ k}\Omega$   $I_N = -45.45 \text{ mA}$ ]



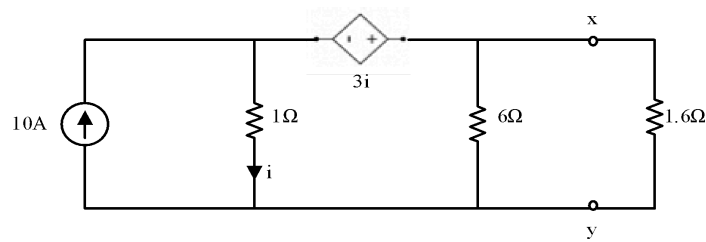
4. Find the current through  $1.6 \Omega$  resistor in the circuit in the below fig. [ Ans:  $6 \text{ A}$ ]



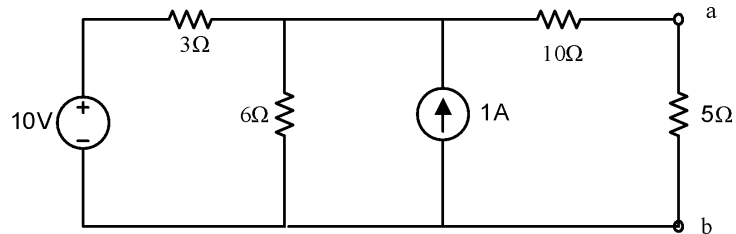
5. Find the current in the  $5\ \Omega$  resistor for the circuit shown in fig. [ Ans:  $I = 509.6\ \text{mA}$  ]



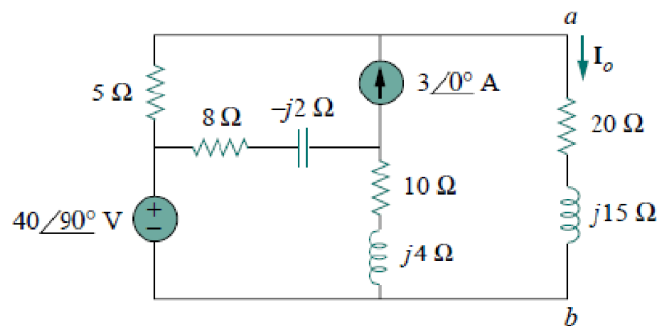6. Obtain current  $I_o$  in Fig. using Norton's theorem.  
[Ans:  $Z_n = 5\ \Omega$ ,  $I_n = (3 + j8\ \text{A})$ ,  $I_o = 1.465 \angle 38.48^\circ\ \text{A}$  ]



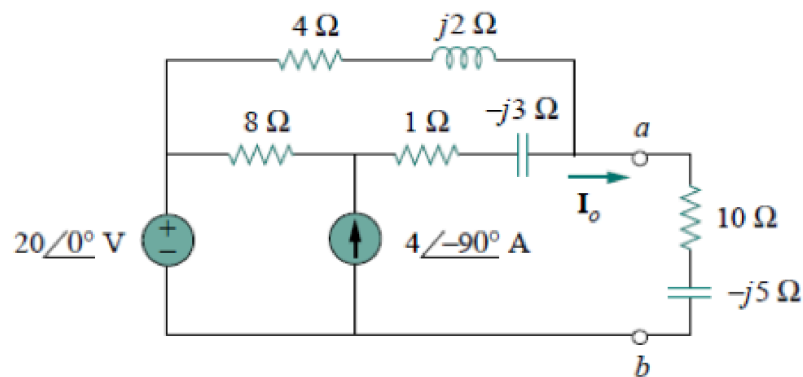7. Determine the Norton equivalent of the circuit in Fig. as seen from terminals a-b. Use the equivalent to find  $I_o$ . [Ans:  $Z_n = 3.176 + j0.706\ \Omega$ ,  $I_n = 8.396 \angle -32.68^\circ\ \text{A}$ ,  $I_o = 1.971 \angle -2.101^\circ\ \text{A}$  ]



8. Show the complete Norton equivalent circuit for the circuit in Figure.  
[Ans:  $I_n = 344 \angle 121^\circ\ \text{mA}$ ,  $Z_n = (24.8 - j28)\ \Omega$  ]

