

National Institute of Technology, Silchar
End-Semester (UG) Examinations, April- 2022

Subject Code: Ec 101
Semester: 1st
Duration: 1.15 hours

Subject: Basic Electronics
Department: ECE, CSE, EE
Total Marks: 30

Attempt any five Questions

- Q1. (a)** Consider a CE circuit using a BJT having $I_s=10^{-15}$ A, a collector resistance $R_c=8.8\text{K}\Omega$, and a power supply of $V_{cc}=12\text{V}$.
- Determine the value of the bias voltage V_{BE} required to operate the transistor at $V_{CE}=5.2\text{V}$. What is the corresponding value of I_c ?
 - Find the voltage gain A_v at this bias point. If an input sine-wave of 5mV peak amplitude is superimposed on V_{BE} , find the amplitude of output sine-wave signal (assume linear operation).
- [3]
- (b)** Simplify the following function F using K map: $F(A,B,C,D)=(0,2,3,5,7,9,11,13,14)$ [3]
- Q2. (a)** A CE amplifier utilizes a BJT with $\beta=100$ and $V_A=100\text{ V}$, is biased at $I_c=1\text{mA}$ and has a collector resistance $R_c=5\text{K}\Omega$. Find R_{in} , R_o and A_{vo} . If the amplifier is fed with a signal source having a resistance of $5\text{K}\Omega$, and a load resistance $R_L=5\text{ K}\Omega$ is connected to the output terminal, find the resulting A_v . [3]
- (b)** Draw the output characteristics of N-channel Enhancement type MOSFET and explain different regions of operation. [3]
- Q3. (a)** Simplify the following Boolean expression into one literal
 $W'X(Z'+YZ)+X(W+Y'Z)$ [3]
- (b)** In the circuit shown in Figure 1, the voltage at the emitter was measured and found to be -0.7V . If $\beta=50$, find I_E , I_B , I_C and V_C . [3]

 


Figure 1

Q4. (a) Find V_{out} of the circuit given in figure 2:

[3]

 


Figure 2


(b) Design a combinational logic circuit with three input variables that will produce a logic 0 as output when more than one input variable are logic 0. [3]

Q5. (a) If the differential amplifier has a differential gain of 20000. CMRR-80dB, then Find the common mode gain. [1]

(b) An OP-AMP has a slew rate of 5 V/usec. Find the largest sine wave output voltage possible at a frequency of 1 MHz. [1]

c) For the circuit as shown in the figure 3, determine the following:

 - i) Drain current I_{DQ} ii) Gate to source voltage V_{GSQ} iii) Drain voltage V_D iv) Source voltage V_s



[4]

Figure 3

Q6. (a) What is the drain current for D-MOSFET having the characteristics of $I_{DSS} = 10\text{ mA}$, $V_{GS(off)} = -4\text{ V}$, and $V_{GS} = 2\text{ V}$. [2]

(b) If $V_1 = 10\sin(200t)$ and $V_2 = 15\sin(200t)$. What is V_{out} ? [4]

